

I. HJERENA NESIGURNOST, multimeter

I.1. SUSTAVNA POGREŠKA

$$\left. \begin{array}{l} R = 100 \Omega \\ R_{MULTIMETAR} = 109,3 \Omega \\ R_{KABELA} = 10 \Omega \end{array} \right\} \Rightarrow R_m = R_k + R \Rightarrow R = 99,3 \Omega$$

↳ sustavna pogreška, možemo ublažiti:

- PROJEKTEM HJERNOG POSTAVA CIJELO DE

→ kraci kabel, manji Rkabela, direktno spajanje ohvata na multimeter, četvero električno mjerjenje

- KOREKCIJOM HJERENJA

I.2. PRECIZNOST I ISKAZIVANJE HJERNOG REZULTATA

$$R = 100 \Omega$$

$$\times \text{različnost} = 0,01 \Omega \quad <109,27, 109,33>$$

$$n = 1000$$

$$P(R) = \frac{1}{\sqrt{2\pi} \cdot \sigma_R} \exp \left[-\frac{1}{2} \left(\frac{R - \bar{R}}{\sigma_R} \right)^2 \right]$$

normalna razdiobaj, preciznost učitava?

$$\bar{R} = \frac{\sum_{i=1}^m N_i \cdot R_i}{\sum_{i=1}^m N_i} = 99,30 \Omega \quad \sigma_R = \sqrt{\frac{1}{N-1} \sum_{i=1}^m (R_i - \bar{R})^2} = 0,01 \Omega$$

POUZDANOST

REZULTAT

$$68,27\% \longrightarrow \bar{R} \pm \sigma_R$$

$$95,45\% \longrightarrow \bar{R} \pm 2\sigma_R$$

$$99,73\% \longrightarrow \bar{R} \pm 3\sigma_R$$

I.3. TOČNOST I RELATIVNA POGREŠKA

$R_m = 99,3 \Omega$: tablica (uniformna gustoća razdiobe)

OPSEG: $200 \Omega \rightarrow$ različnost: $0,1 \Omega \rightarrow$ TOČNOST: $\pm (0,8\% + 3 \text{ digita})$

VJEĆEDNOST SE 100% nalazi u intervalu $\boxed{\bar{R} \pm 9}$

$$\pm (x\% + y \text{ digita}) \Rightarrow a = \frac{x}{100} \cdot R + y \cdot r$$

$$a = \frac{0,8}{100} \cdot 99,3 + 3 \cdot 0,1 = 1,1 \Omega \Rightarrow \boxed{(99,3 \pm 1,1) \Omega}$$

RELATIVNA
POGREŠKA

$$P = \frac{|HJERENO - REF|}{REF} \cdot 100\% = \frac{99,3 - 100}{100} \cdot 100\% = -0,7\%$$

1.4. SLOŽENA MJEĐNA NESIGURNOST I KORELACIJA

* 2 multimetera → I. način → koristimo samo 1 $r=1$! → VAŽNO
 * 2 multimetera → II. način → koristimo oba $r=\emptyset$! → * u stvarnosti
 * u stvarnosti
 nizad nije
 nizad nije

jeftinalih značajki, kježi utječe na manju nesigurnost?

$$U = 100,0 \text{ V} \quad \sigma_1 = u(U) = 0,2 \text{ V}$$

$$I = 1,00 \text{ A} \quad \sigma_2 = u(I) = 0,01 \text{ A}$$

$$\sigma_y = \sqrt{\sum_{i=1}^m \left(\frac{\partial f}{\partial x_i} \right)^2 \sigma_i^2 + 2 \cdot \sum_{i=1}^{m-1} \sum_{j=i+1}^m \frac{\partial f}{\partial x_i} \frac{\partial f}{\partial x_j} \Gamma(x_i, x_j) \sigma_i \sigma_j}$$

$$\Gamma(\sigma_i, \sigma_j) = \frac{\text{cov}(x_i, x_j)}{\sigma_i \cdot \sigma_j}$$

I. način

$$\sigma_{P1} = \sqrt{I^2 \cdot \sigma_u^2 + U^2 \cdot \sigma_I^2 + 2 \cdot I \cdot U \cdot \sigma_I \cdot \sigma_u} = 1,4 \text{ W}$$

$$\text{II. način} \Rightarrow \sigma_{P2} = \sqrt{I^2 \cdot \sigma_u^2 + U^2 \cdot \sigma_I^2} \approx 1,1 \text{ W} \rightarrow \text{Boyle} \quad (200,00 \pm 1,1) \text{ W}$$

1.5. ZADACI

1. $P \rightarrow$ nekolikratnim mjerenuju u i R

$$\sigma_u = 0,05 \text{ V}$$

$$U = 1900 \text{ V}$$

$$\sigma_R = 0,07 \text{ } \Omega$$

$$R = 20,00 \Omega$$

$$\sigma_P = \sqrt{\left(\frac{2U}{R}\right)^2 \cdot \sigma_u^2 + \left(-\frac{U^2}{R^2}\right)^2 \cdot \sigma_R^2 + 2 \sum_{i=1}^{n-1} \sum_{j=i+1}^n \Gamma(x_i x_j) \sigma_i \sigma_j}$$

$$= 0,053 \text{ W}$$

$$P = \frac{U^2}{R} = 5 \text{ W}$$

$$\underline{P = (5,000 \pm 0,053) \text{ W}}$$

2. $R_1 = 1200 \Omega \quad \sigma_{R_1} = 5 \Omega \quad (\text{jedan multimeter})$

$R_2 = 2500 \Omega \quad \sigma_{R_2} = 7 \Omega \quad (\text{drugi multimeter})$

$$\Gamma(R_1, R_2) = \underline{0,371}$$

$$R = R_1 + R_2 = 3700 \Omega$$

$$R = (3700 \pm 10) \Omega$$

$$\sigma_R = \sqrt{\sigma_{R_1}^2 + \sigma_{R_2}^2 + 2 \cdot 0,371 \cdot 5 \cdot 7} = 10 \Omega$$

3. $\boxed{P = U \cdot I}$ (jedan multimeter $\Rightarrow \Gamma = 1$)

$$\begin{cases} I = 2,5 \text{ A} \\ U = 160 \text{ V} \end{cases} \quad \text{tablica}$$

$$\xrightarrow{\text{za } I} \text{M.O.} = 4 \text{ A} \rightarrow \Gamma = 0,001 \text{ A} \rightarrow \pm (2,5\% + 5)$$

$$\begin{aligned} \sigma_I &= \alpha_1 = \frac{2,5}{100} \cdot 2,5 + 5 \cdot 0,001 \text{ A} \\ &= 0,0675 \text{ A} \end{aligned}$$

$$\xrightarrow{\text{za } U} \text{M.O.} = 500 \text{ V} \rightarrow \Gamma = 100 \text{ mV} \rightarrow \pm (1\% + 5)$$

$$\sigma_U = \alpha_2 = \frac{1}{100} \cdot 160 + 0,1 \cdot 5 = 2,1 \text{ V}$$

$$\sigma_P = \sqrt{I^2 \sigma_U^2 + U \cdot \sigma_I^2 + 2 \cdot U \cdot I \cdot 1 \cdot \sigma_I \cdot \sigma_U} = 16 \text{ W}$$

$$\underline{P = (400 \pm 16) \text{ W}}$$

$$4. U_{DC} = 4 \text{ V}$$

$$U_{AC,ref} = 3 \text{ V}$$

sinus

a) za DC

$$U = 4 \text{ V}$$

$$U_{DC} = (4,000 \pm 0,033) \text{ V}$$

$$\sigma_{DC} = \frac{0,08}{100} \cdot 4 + 0,001 = 0,033 \text{ V}$$

b) za AC

$$U = 3 \text{ V}$$

$$5 \text{ V}$$

$$U_{AC} = (3,000 \pm 0,035) \text{ V}$$

$$\sigma_{AC} = \frac{1}{100} \cdot 3 + 5 \cdot 0,001 = 0,035 \text{ V}$$

$$\boxed{U_{ef} = \sqrt{U_{DC}^2 + U_{AC,ref}^2} = 5 \text{ V}}$$

5. dva multimetra \Rightarrow nizimo R

prvi mult. drugi mult.

$$U_{\text{el}} = 9,40 \text{ V} \quad I_{\text{el}} = 9,00 \text{ mA}$$

$$\Omega_1 = 0,04 \text{ V}$$

$$\Omega_2 = 0,01 \text{ m}\Omega$$

$$r = -0,15$$

$$R = \frac{U}{I}$$

$$\Omega_R = \sqrt{\left(\frac{1}{I}\right)^2 \cdot \Omega_1^2 + \left(-\frac{U}{I^2}\right)^2 \cdot \Omega_2^2 + 2 \cdot \frac{1}{I} \cdot \frac{-U}{I^2} \cdot (-0,15) \cdot \Omega_1 \cdot \Omega_2}$$

2 mult

$$= 8,6 \text{ }\Omega$$

$$R_{\text{jedn}} = 1,076 \text{ }\Omega$$

mult

$$\Omega_R = \frac{1}{100} \cdot 1076 + 2 \cdot 1 = 12,76 \Omega = 13 \Omega$$

$$R_{\text{STVARVO}} = 1079,000 \Omega$$

dva mult: $R = (1080 \pm 8,6) \Omega \rightarrow$ točnije

jedan mult: $R = (1076 \pm 13) \Omega$

$$6. U_{\Delta C_1} = 250,3 \quad M.P. = 400 \text{ mV} \quad \Rightarrow \quad \Omega_1 = a_1 = \frac{0,8}{100} \cdot 250,3 + 3 \cdot 0,1 = 2,3024 \text{ mV} = 2,3 \text{ mV}$$

$$U_{\Delta C_2} = 0,250 \quad M.P. = 4 \text{ V} \quad \Rightarrow \quad \Omega_2 = a_2 = \frac{0,8}{100} \cdot 0,250 + 1 \cdot 0,001 = 0,003 \text{ V}$$

preciznije

$$7. U_{\text{el}} = 3 \sin(2\pi ft) + 3 \text{ [V]}$$

$$G_{AC} = \pm (1\% + 5 \text{ znamenki})$$

$$G_{DC} = \pm (0,8\% + 1 \text{ znamenka})$$

$$U_{\Delta C} = 3 \text{ V}$$

$$U_{AC} = U_{ef} = \frac{U_m}{\sqrt{2}} = 2,121 \text{ V}$$

$$G_{DC} = \Omega_{DC} = \frac{0,8}{100} \cdot 3 + 1 \cdot 0,001 = 0,025 \text{ V}$$

$$G_{AC} = \Omega_{AC} = \frac{1}{100} \cdot 3 + 5 \cdot 0,001 = 0,035 \text{ V}$$

zamešnjivo

$$U_{ef} = \sqrt{U_{DC}^2 + U_{AC}^2}$$

$$U_{ef, \min} = 3,639 \text{ V}$$

$$U_{ef, \max} = 3,710 \text{ V}$$

8.

3. ELECTROMAGNETSKE SMETNJE

3.1. ASIMETRIČNI SPOJ

$$l_{kabel} = 5 \text{ m}$$

$$R = 1 \text{ k}\Omega$$

Iznos simetrične uslijed kapacitivnog vremenja kabla s udomu graditelje nute? zadana


$$C_k = 100 \text{ pF/m} \cdot 5 \text{ m} = 500 \text{ pF}$$

$$C_R = 10 \text{ pF}$$

$$R_V = 1 \text{ M}\Omega$$

$$C_V = 25 \text{ pF}$$

otpor mreže \Rightarrow

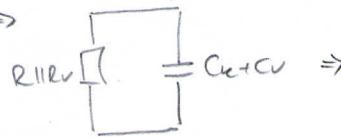

999 n

$$\frac{(R_V \parallel R) \cdot \left(\frac{1}{j\omega(C_k + C_V)} \right)}{R_V \parallel R + \frac{1}{j\omega(C_k + C_V)}} = \frac{999}{j\omega 5,24475 \cdot 10^{-7} + 1}$$

otpor mreže

$$= \frac{999}{1 + j\omega 5,24475 \cdot 10^{-7}}$$

$$\frac{1}{j\omega C_k} + \text{otpor mreže} = \frac{1 + j\omega 10 \cdot 10^{-12}}{1 + j\omega 10 \cdot 10^{-12}} = \omega^2 \cdot 5,24475 \cdot 10^{-18}$$


$$\Rightarrow \frac{R_V \parallel R}{1 + j\omega(C_k + C_V)(R_V \parallel R)} \Rightarrow$$

$$\frac{\frac{R_V \parallel R}{1 + j\omega(C_k + C_V)(R_V \parallel R)}}{\frac{1}{j\omega C_k} + \frac{R_V \parallel R}{1 + j\omega(C_k + C_V)(R_V \parallel R)}}$$

$$= \frac{\frac{R_V \parallel R}{1 + j\omega(C_k + C_V)(R_V \parallel R)}}{\frac{(1 + j\omega(C_k + C_V)(R_V \parallel R)) + R_V \parallel R \cdot j\omega C_R}{(1 + j\omega(C_k + C_V)(R_V \parallel R)) \cdot (j\omega C_R)}}$$

$$= \boxed{\frac{j\omega C_R(R_V \parallel R)}{1 + j\omega(C_k + C_V + C_R)(R_V \parallel R)}} = X$$

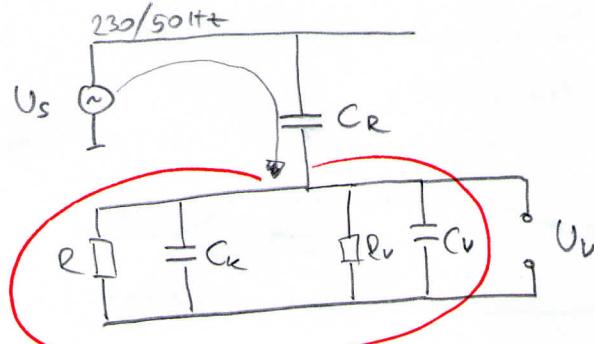
$$U_V = U_S \cdot X = 7,2184 \cdot 10^{-4} \text{ V} = 0,722 \text{ mV}$$



$$U_V = U_S \cdot \frac{\text{otpor mreže}}{\text{otpor mreže}}$$

$$\frac{1}{j\omega C_k} + \text{otpor mreže}$$

3.2. DIFERENCIJALNI SPOJ

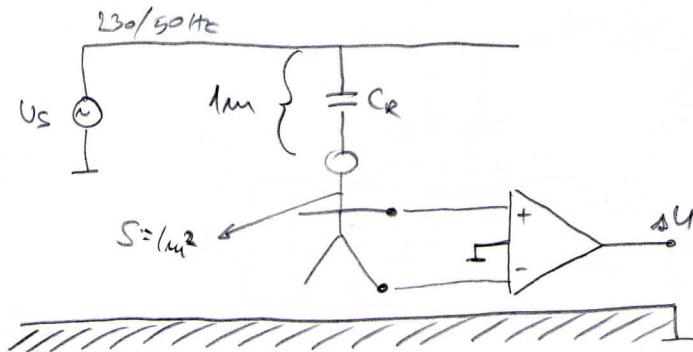

$$Cr = E_0 \cdot \frac{f}{2} = 8,854 \cdot 10^{-12} \frac{V}{A} \cdot \frac{1}{2\pi f} = 8,854 \mu F$$

$$U_z = U_s \cdot \left| \frac{R_{most}}{\frac{1}{j\omega C_e} + R_{most}} \right|$$

$$= U_s \cdot \left| \frac{j\omega C_e R_{most}}{1 + j\omega C_e R_{most}} \right| = U_s \cdot \frac{\omega C_e R_m}{\sqrt{1^2 + \omega^2 C_e^2 R_m^2}} =$$

| = 3,2 V | napon simetrije

↳ R_{E1} i R_{E2} nisu isti pa će se ta svestrjava pogoditi na izlazu



$$\Delta U = U_z \cdot \left(\frac{R_z}{R_{E1} + R_z} - \frac{R_z}{R_{E2} + R_z} \right) = 0,637 \text{ mV}$$

* ako je $R_{E1}, R_{E2} \ll R_z \Rightarrow \Delta U \approx U_z \cdot \frac{R_{E1} - R_{E2}}{R_z} = 640 \mu V$

→ uva par rješenja za ovaj problem, ali najbolje je


PLIVAJUĆE POJACALO

→ povećavanje impedancije R_z

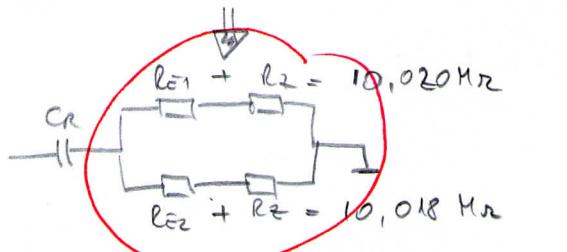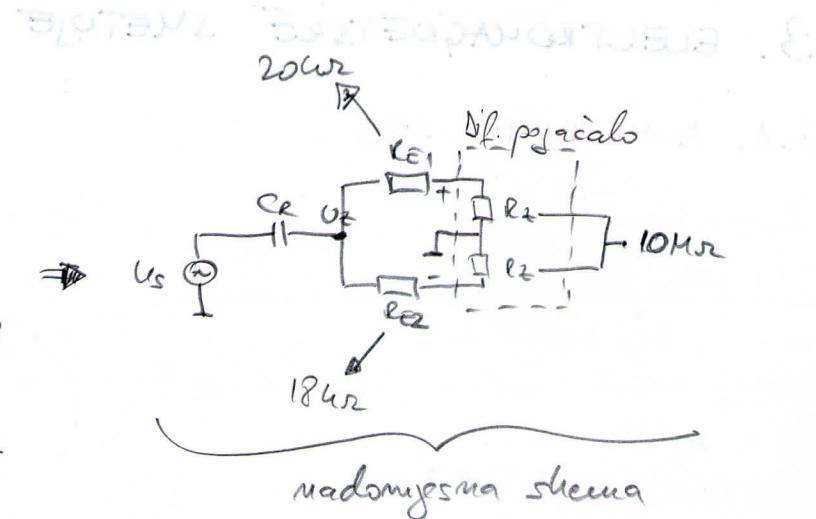

most $R_{most} = R \parallel R = 5,0095 \text{ Hz}$

3.3. PCLIVAJUĆI SPOJ

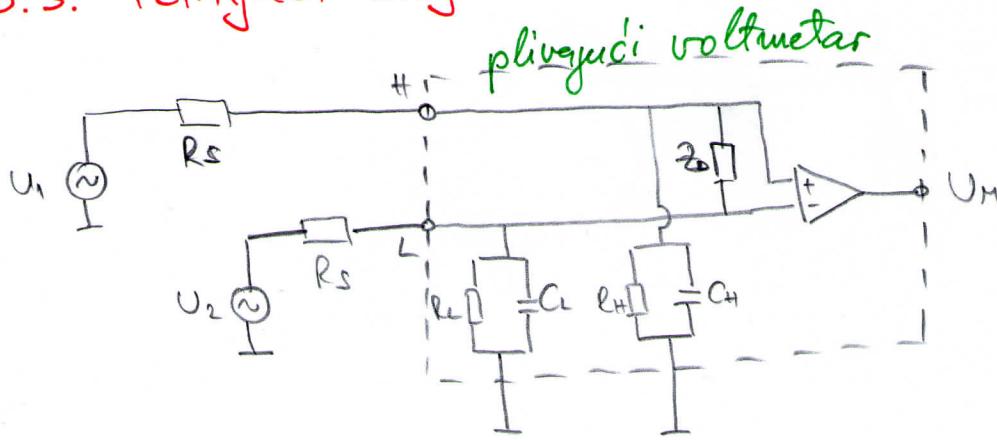

$$Z_H = 2G_{d2} \parallel R_{pf}$$

$$Z_L = 1G_{d2} \parallel 10\text{pF}$$

$$|U_2(\text{sučinj})| < 100\mu\text{V}$$

50 Hz
1000 Hz
10 kHz
100 kHz

$$R_S = 100\Omega, Z_0 = \infty$$

$$U_M = U_H - U_L = U_1 \cdot \frac{Z_H}{R_S + Z_H} + U_2 \cdot \frac{Z_L}{R_S + Z_L}$$

$$\Rightarrow \frac{1}{2} \left[\frac{Z_H}{Z_H + R_S} + \frac{Z_L}{Z_L + R_S} \right] (U_1 - U_2) + \left[\frac{Z_H}{Z_H + R_S} - \frac{Z_L}{Z_L + R_S} \right] \frac{U_1 + U_2}{2}$$

KONTROLA

diferencijalni
napon

SMETNA

zajednički
napon

$$Z_H, Z_L \gg R_S$$

dif. pojačanje teži $\rightarrow 1$

zajedničko pojačanje teži $\rightarrow \emptyset$

princip
radu
plivajućeg
pojedala

$$\text{UVJET: } \left(\frac{Z_H}{Z_H + R_S} - \frac{Z_L}{Z_L + R_S} \right) \cdot U_2 \leq 100\mu\text{V}$$

$$Z_H = \frac{R_H \cdot \frac{1}{j\omega C_H}}{R_H + \frac{1}{j\omega C_H}} = \frac{R_H}{1 + j\omega C_H R_H}$$


$$Z_L = \frac{R_L}{1 + j\omega C_L R_L}$$

f	$U_{2,\text{max}} [\text{V}]$
50 Hz	1245
1 kHz	80
10 kHz	8
100 kHz	0.8

FACTOR POTISKIVANJA:

omjer pojačanja dif. signala i pojačanja zajedničkog signala
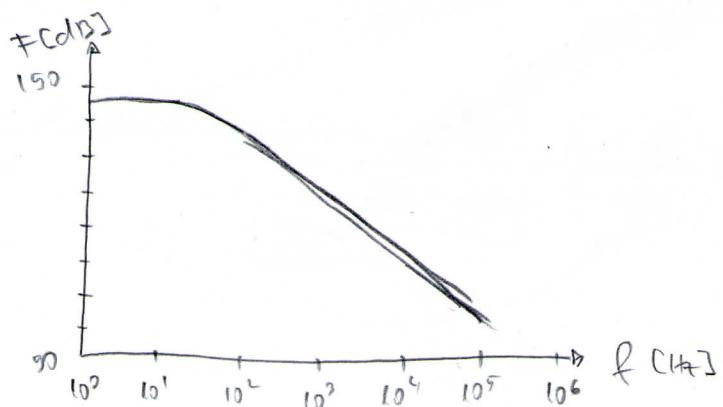
$$F = \frac{\frac{1}{2} \left(\frac{Z_H}{Z_H + R_S} + \frac{Z_L}{Z_L + R_S} \right)}{\left(\frac{Z_H}{Z_H + R_S} - \frac{Z_L}{Z_L + R_S} \right)}$$




3.4. ZADACI

$$\textcircled{1} \quad L = 10 \text{ mH}$$

$$U_1 = 230 \text{ V}$$

$$U_S < 2,2 \text{ mV}$$

Oba vodiča $d = 1 \text{ mm}$

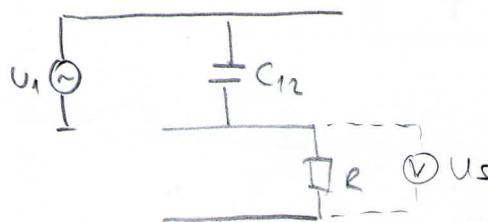

$$C_{12} = \frac{\pi \cdot \epsilon_0}{\ln(2D/d)} (2D/d)$$

$$D = ?$$

$$U_S = U_1 \cdot \frac{R}{R + C_{12}} = \frac{j\omega C_{12} \cdot R}{1 + j\omega C_{12} \cdot R} = \frac{\omega C_{12} \cdot R}{\sqrt{1^2 + \omega^2 \cdot C_{12}^2 \cdot R^2}}$$

$$U_S < 2 \text{ mV} \Rightarrow U_S = U_1 \cdot \frac{2\pi f \cdot 10000 \cdot \frac{\pi \epsilon_0}{\ln(2D/d)}}{\sqrt{1^2 + \omega^2 \cdot C_{12}^2 \cdot 10000^2}} \Rightarrow C_{12} = \frac{U_S}{U_1} \cdot \frac{1}{\omega \cdot R} = 3,0447 \cdot 10^{-12} \text{ F}$$

$$C_{12} = \frac{\pi \cdot \epsilon_0}{\ln(2D/d)} \Rightarrow \ln(2D/d) = \frac{\pi \cdot \epsilon_0}{C_{12}} / e$$

$$\frac{2D}{d} = e^{\frac{\pi \cdot \epsilon_0}{C_{12}}} \Rightarrow D = \frac{d}{2} e^{\frac{\pi \cdot \epsilon_0}{C_{12}}} = 4,64 \text{ mm}$$

$$\textcircled{2} \quad 2\pi f = 10 \text{ MHz} \parallel 20 \text{ pF}$$


ASIMETRIČAN UZI \rightarrow jedna polulijanica na masi

$$C_R = 5 \text{ pF}$$

$$R_g = ? \quad U_S < 50 \mu\text{V} \quad (\text{visina menjavost})$$

$$230/\sqrt{2} \parallel$$

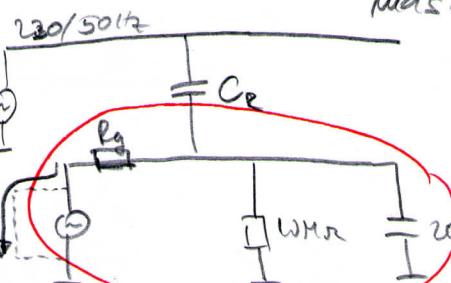metoda superpotencije
* zemlja nema samo
utjecaj gradišne nivoze



$$Z = \frac{R_g \parallel R_v \cdot \frac{1}{j\omega C_v}}{R_g \parallel R_v + \frac{1}{j\omega C_v}} = \frac{R_g \parallel R_v}{1 + j\omega C_v R_g \parallel R_v}$$

$$= \frac{R_g \cdot R_v}{R_g + R_v + j\omega C_v \cdot R_g + R_v}$$

$$U_S = U_1 \cdot \frac{Z}{Z + \frac{1}{j\omega C_v}} = \frac{j\omega C_v \cdot R_g \cdot R_v}{R_g + R_v + j\omega C_v \cdot R_g + R_v + j\omega C_v \cdot \frac{1}{R_g \parallel R_v}}$$

$$Z + \frac{1}{j\omega C_v} = \frac{R_g \parallel R_v + j\omega C_v \cdot R_g + R_v + j\omega C_v \cdot \frac{1}{R_g \parallel R_v}}{j\omega C_v \cdot (R_g + R_v + j\omega C_v \cdot R_g + R_v)}$$

$$\frac{U_S}{U_1 \sqrt{2}} = \frac{w \cdot C_v \cdot R_g \cdot R_v}{\sqrt{(R_g + R_v)^2 + (w(R_g \cdot C_v \cdot R_v) + wC_v \cdot R_g \cdot R_v)^2}}$$

zamjenjujemo

$$\frac{w C_v \cdot R_g \cdot R_v}{R_g + R_v}$$

$$\Rightarrow R_g = \frac{-R_v}{\left(1 - \frac{U_S}{U_1 \sqrt{2}} w \cdot C_v \cdot R_g \cdot R_v\right)} = 97,86 \text{ M}\Omega$$

③ asimetrický už

$$R_{ul} = 10 \text{ M}\Omega$$


$$C_1 = 5 \text{ pF}$$

$$C_2 = 5 \text{ pF}$$

$$C_3 \gg C_1 + C_2$$

\Rightarrow
zameňujeme

C_3

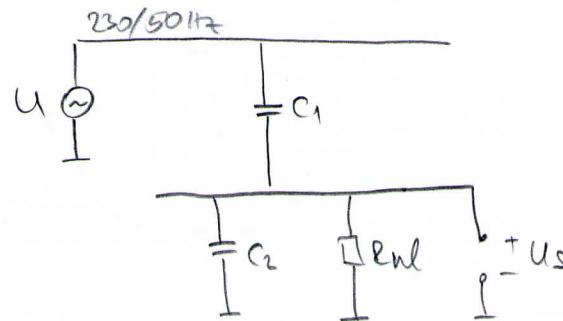

$$U_s = U \cdot \frac{\frac{R_{ul}}{1 + j\omega C_1 \cdot R_{ul}}}{\frac{1}{j\omega C_1} + \frac{R_{ul}}{1 + j\omega C_2 \cdot R_{ul}}} = \frac{j\omega C_1 \cdot R_{ul}}{1 + j\omega C_2 \cdot R_{ul} + j\omega R_{ul} \cdot C_1} \cdot U$$


$$U_s = U \cdot \frac{\omega C_1 \cdot R_{ul}}{\sqrt{1^2 + (\omega(C_2 \cdot R_{ul} + C_1 \cdot R_{ul}))^2}} = 3,61 \text{ V}$$

zameňujeme

$$\text{④ sonda } \times 1 \rightarrow U = 1 \text{ V}, f = 1 \text{ MHz} \quad R_g = 1 \text{ k}\Omega$$

$$\begin{aligned} l_{sonde} &= 1,5 \text{ m} \\ C_{sonde} &= 60 \text{ pF/m} \end{aligned} \Rightarrow C_{sonde} = 90 \text{ pF}$$
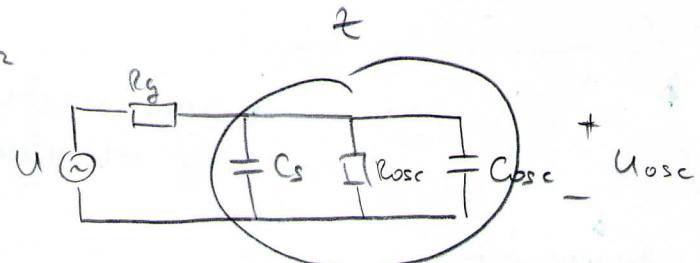
$$Z_{ul} = 1 \text{ M}\Omega \parallel 30 \text{ pF}$$



$$Z = \frac{Rosc \cdot \frac{1}{j\omega(C_s + C_{osc})}}{Rosc + \frac{1}{j\omega(C_s + C_{osc})}} = \frac{Rosc}{1 + j\omega(C_s + C_{osc}) \cdot Rosc}$$

$$\begin{aligned} U_{osc} &= U \cdot \frac{Z}{Z + R_g} = \frac{Rosc}{Rosc + R_g + j\omega(C_s + C_{osc})Rosc \cdot l_g} \cdot U \\ &= \frac{Rosc \cdot U}{\sqrt{(Rosc + R_g)^2 + (\omega(C_s + C_{osc})Rosc \cdot l_g)^2}} = 0,7 \end{aligned}$$

zameňujeme


$$⑤ A_D = 100$$

$$R_{UL} = 1 \text{ M}\Omega$$


$$R_1 = R_2 = R_3 = R_4 = 10 \text{ k}\Omega$$

$$C_{ULop}/w_0 = 160 \text{ pF}$$



$$C_{ULop}/w_{res} = 200 \text{ pF}$$

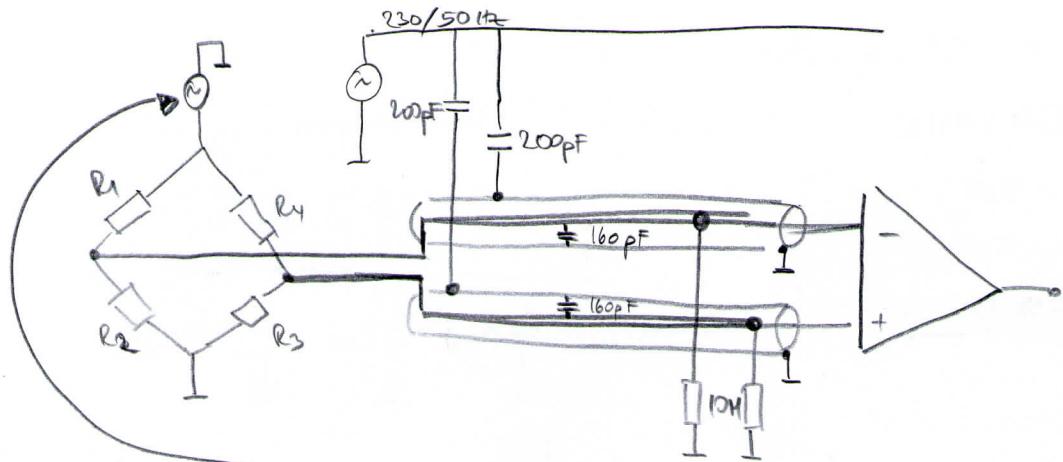

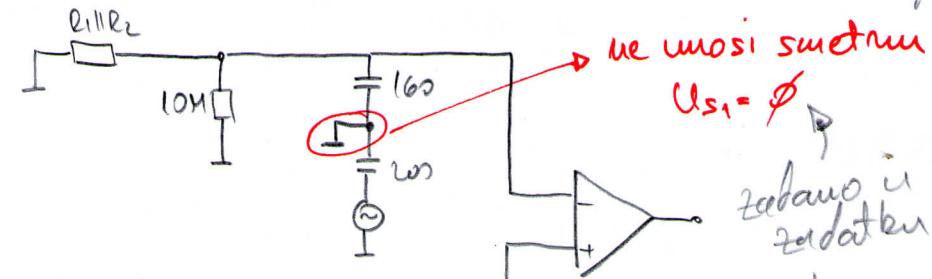* taipuva mas samo simetrija pa itinor kretko spajomis


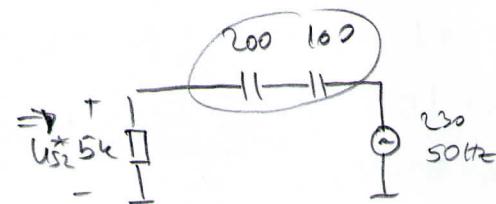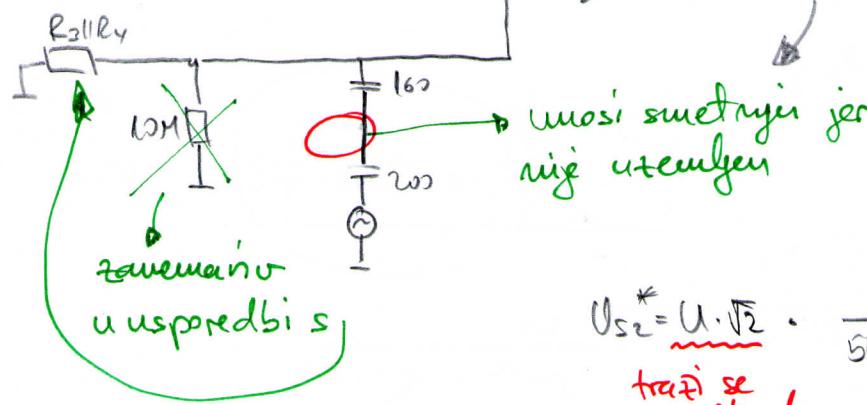
$$C_{UL} = \frac{C_1 \cdot C_2}{C_1 + C_2} = 88,88 \text{ pF}$$



$$U_{S2}^* = U \cdot \sqrt{2} \cdot \frac{5\text{n}}{5\text{n} + jwC_{UL}} = U \cdot \sqrt{2} \cdot \frac{jwC_{UL} \cdot 5\text{n}}{1 + jwC_{UL} \cdot 5\text{n}} = 0,045 \text{ V}$$

$$U_{S2} = A_D \cdot U_{S2}^* = 4,5 \text{ V}$$


⑥ plivajući ulaz \Rightarrow voltmeter

$$F = ? \quad U_2 = 50V$$

$$R_g = 1M\Omega$$

$$R_1 = 2G\Omega$$

$$R_2 = 1.5\Omega$$

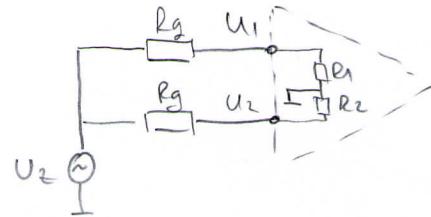

pojačanje $\times 1$

$$U_{12} = A(U_1 - U_2)$$

$$U_1 = U_2 \cdot \frac{R_1}{R_g + R_1} = 49,999975 V \quad \left. \right\} \Delta U = U_1 - U_2 = 8,33 \cdot 10^{-6} V$$

$$U_2 = U_2 \cdot \frac{R_2}{R_g + R_2} = 49,99996667 V$$

$$\boxed{F = \frac{A \Delta}{A_2} = \frac{\frac{U_{12}}{U_{12}}}{\frac{U_{12}}{U_{12}}} = \frac{1}{\frac{(U_1 - U_2) \cdot A}{U_2}} = \frac{U_2}{\Delta U} = 6000015,936 \Rightarrow 135 dB}$$

4. SENZORI

4.1. PIEZOELEKTRICKÝ SENSOR SÍLÉ

$$\epsilon_r = 5, \quad S = 1,5 \text{ cm}^2, \quad d = 1,5 \text{ mm}, \quad \alpha = 0,1 \text{ pC/N}$$

$$l_k = 5 \text{ m}, \quad C_k = 80 \text{ pF/m}$$

$$Z_v = 10 \text{ M}\Omega \parallel 12 \text{ pF}$$


Macrtaj silemu, $f_dg = ?$

$F = ?$ also $t = 2,5 \text{ ms} \rightarrow U_v = 375 \text{ mV}$

$$C_g = \epsilon_0 \cdot \epsilon_r \cdot \frac{S}{d} = 4,427 \text{ pF}$$

$$C_k = l \cdot C_k^* = 400 \text{ pF}$$


→ največia pa najvišie učinkovitá f_dg

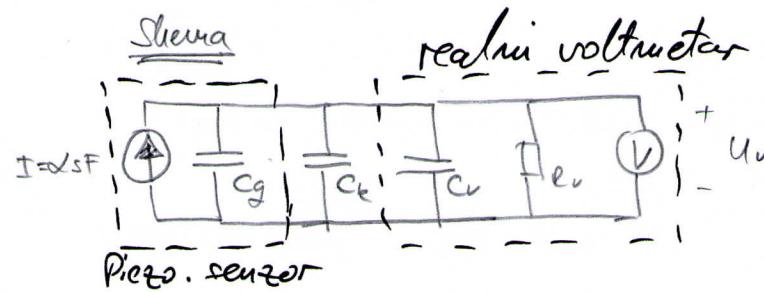

$$U_v = I \cdot Z_{kulupivo} = \alpha \cdot F(s) \cdot \frac{\frac{1}{R_v + \frac{1}{s(C_g + C_k + C_v)}}}{\frac{1}{R_v + \frac{1}{s(C_g + C_k + C_v)}}} = \alpha \cdot s \cdot F(s) \cdot \frac{R_v}{1 - s(C_g + C_k + C_v) \cdot R_v}$$

$$f_d = \frac{\omega}{2\pi} = \frac{1}{2\pi \cdot C} = \frac{1}{2\pi} \cdot \frac{1}{(C_k + C_g + C_v) \cdot R_v} = 32,35 \text{ Hz}$$
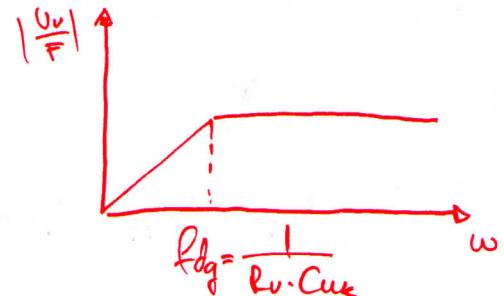
$$F(s) = \frac{F_0}{s} \rightarrow \text{konstantná sila } \text{u } t=0+$$



$$U_v(s) = \frac{\alpha \cdot F_0}{(C_g + C_k + C_v)} \cdot \frac{1}{s + \frac{1}{RC}} \rightarrow U_v(t) = \frac{\alpha \cdot F_0}{(C_g + C_k + C_v)} \cdot \exp\left(-\frac{t}{RC}\right)$$

$$U_v(t=2,5 \text{ ms}) = 375 \text{ mV} \rightarrow F_0 = 2,846 \text{ N}$$

4.2. TEMP. SENSOR U MOSTOVOM SPREJMU → mjeri u ispitu

BRDZIĆ A.

$$\alpha = 3,96 \cdot 10^{-3} \text{ 1/}^{\circ}\text{C}$$

$$R_0 = 100\Omega \quad (T=0^{\circ}\text{C})$$

$$R_1 = R_2 = R_4 = R = 100\Omega$$


$$U = 5V$$

$$A_D = 20 \text{ dB} = 10$$

$$F = 100 \text{ dB} = 100000$$

$$U_{1\text{z}} (T=50^{\circ}\text{C}) = ?$$

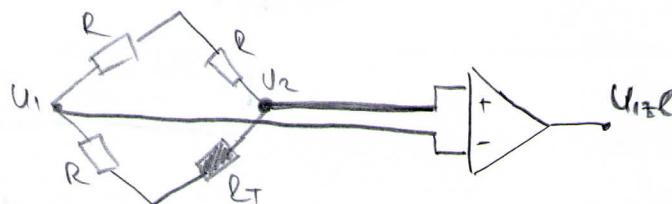↳ tačko most a ne obični R ?
↳ veća osetljivost



$$R_T = R_0 (1 + \alpha \cdot \Delta T) = 100 \cdot (1 + 3,96 \cdot (50^{\circ}\text{C} - 0^{\circ}\text{C})) = 119,8 \Omega$$

$$U_1 = U \cdot \frac{R}{R+R} = 2,5 \text{ V} \quad \left. \right\} \Rightarrow U_2 = \frac{U_1 + U_2}{2} = 2,6126 \text{ V}$$

$$U_2 = U \cdot \frac{R_T}{R+R_T} = 2,7252 \text{ V}$$

$$\Delta U = U_2 - U_1 = 0,2252 \text{ V}$$

$$F = \frac{A_D}{A_Z} \Rightarrow A_Z = \frac{A_D}{F} = 1 \cdot 10^{-4}$$

\downarrow
 $u \text{ dB}$

$$U_{1\text{z}}(l) = \Delta U \cdot A_D \pm U_2 \cdot A_Z$$

$$\Delta A_Z \text{ dB} = A_D \text{ dB} - F \text{ dB} = -80 \text{ dB}$$

$$= 2,25200 \pm 0,00026 \text{ V}$$

4.3. INDUCTIVNI SENZOR POMAKA S PROMJENOM REKULTANCije

* ispitni

jako precizan senzor pomaka

$$l = 4,7 \text{ cm}$$

$$U_{sin} = 5 \text{ V}, f = 20 \text{ kHz}$$

$$d = 2 \text{ mm}$$

$$x=0 \Rightarrow [I_L = 3 \cdot I_E] \text{ uvjet?}$$

broj naviota?

$$\text{presek jeuge } 2 \text{ cm}^2 \text{ i } [\mu_r \gg 1]$$

$$\Delta U = 70 \text{ mV}, x=?$$

→ prelak od ravnotežnog položaja

Ampersov zakon

$$L = \frac{N^2}{\frac{l_m}{\mu_0 \mu_r S} + \frac{L_d}{\mu_0 \cdot S}}$$

zamenujemo jer ulupin put kroz maki koji su u sag. točki prođe dve se ne zatvaraju kroz zavoj zavojnice


parni presjek je prek

rekultancija

$$\text{aproximacija: } L = \mu_0 \cdot N^2 \cdot S \frac{1}{2s}$$

$$\frac{\Delta L}{x} \approx \frac{dL}{ds} = -\mu_0 N^2 S \frac{1}{2s^2} = -\frac{L}{s} \Rightarrow \boxed{\frac{\Delta L}{L} = -\frac{x}{s}}$$
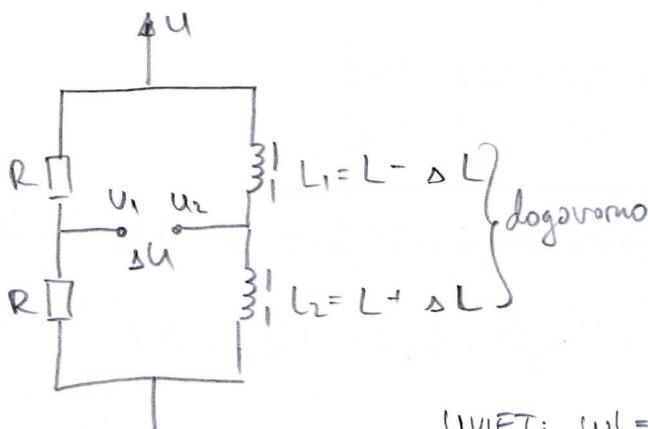
$$\Rightarrow \frac{\Delta L_1}{L_1} = -\frac{\Delta L_2}{L_2}$$




$$\frac{\Delta U}{U} = \frac{j\omega L_2}{j\omega(L_1+L_2)} - \frac{1}{2} = \frac{L_2 \Delta L}{2L} - \frac{1}{2} = \boxed{\frac{\Delta L}{2L}}$$

$$\frac{\Delta L}{2L} = \frac{x}{2s}$$

$$\text{UVJET: } \omega L = \frac{R}{3} \quad (\text{3 puta veća struja} \Rightarrow 3 \times \text{manji otpor})$$

$$L = \frac{R}{3\omega} = 12.46 \text{ mH} \Rightarrow N = \sqrt{\frac{L \cdot 2s}{\mu_0 \cdot S}} = 445$$
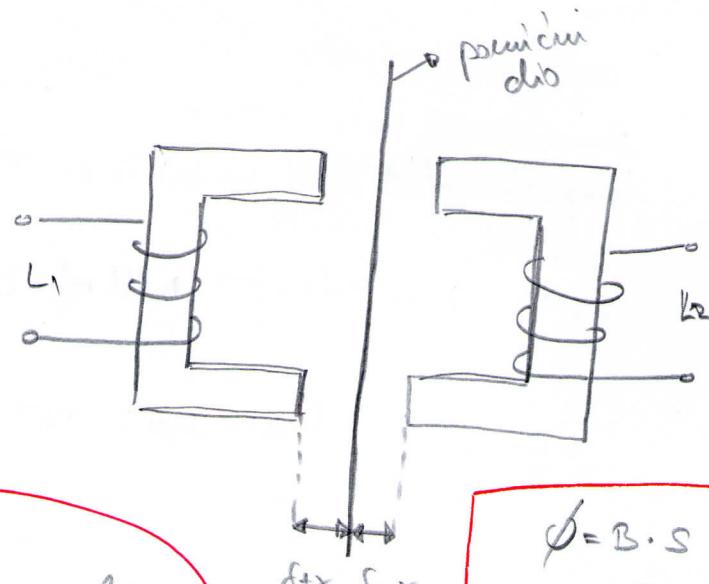
$$\Delta U = 70 \text{ mV} \Rightarrow \frac{\Delta U}{U} = \frac{x}{2s} \Rightarrow x = \underline{\underline{56 \mu\text{m}}}$$



$$\phi = B \cdot S$$

$$N \cdot I = \phi H d l$$

$$N \cdot I = B_0 \left(\frac{l_m}{\mu_0 \mu_r} + \frac{2s}{\mu_0} \right)$$

$$B = \frac{\phi}{S} \Rightarrow L = \frac{N \cdot \phi}{I}$$

4.4. HALLOU SENZOR

↳ ne proizvodi ul. mag. polje

treba mijenjati $\pm 10A$

Hallov senzori: osjetljivost 300 V/T

lin. područje rada $\pm 5 \mu\text{T}$

mag. ekivalent max. iznosa struja $75 \mu\text{T} = B_{\min}$

$$U = +5 \text{ V}$$

$$U_{12} = 2,5 \text{ V} \rightarrow \text{polje} = 0 \text{ T} \Rightarrow U_{\text{ref}} = 2,5 \text{ V}$$

$$A_D = 20 \text{ dB}$$

$$F = 100 \text{ dB}$$

mag. smjeruje do $1 \mu\text{T}$


$$U_{12} = \text{OSJETLJIVOST} \cdot \text{POLE} + \boxed{U_{\text{ref}}}$$

služi da bi mogli mijenjati i negativne vrijednosti

$$U_1 = S \cdot B + U_{\text{ref}}$$

$$\Delta U = \text{kod izlaznog mjenja} = S \cdot \Delta B = 300 \text{ V/T} \cdot (\pm 5 \mu\text{T}) = \pm 1,5 \text{ V}$$
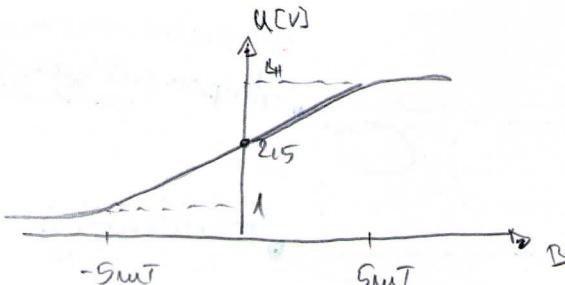
$$U_{12} = U_{\text{ref}} + \Delta U = 2,5 \pm 1,5 \text{ V}$$




* za mijenjajuće jakosti struje Hallovim senzorom, vod mora biti na točno određenoj udaljenosti kako bi se postigla veza između struje i mag. polja koje senzor mijeni

$$B = \mu_0 \cdot \frac{I}{2\pi r} \Rightarrow r = \mu_0 \cdot \frac{S \cdot \Delta I}{2\pi \cdot \Delta U} = 1 \text{ mm}$$

$$\text{zbog sume} \Rightarrow I_{\min} \geq \frac{2\pi r B_{\min}}{\mu_0} = 0,375 \text{ A}$$

potiskivanje mag. smjeruje:

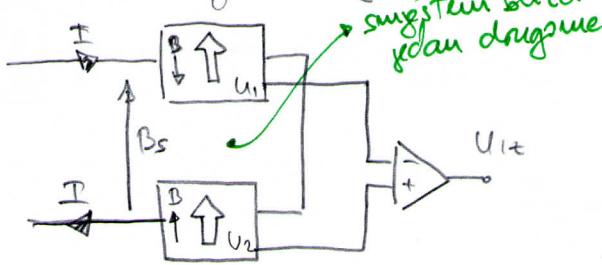

$$U_1 = -BS + B_S S + U_{\text{ref}}$$

$$U_2 = BS + B_S S + U_{\text{ref}}$$

$$U_D = U_2 - U_1 = 2BS = 2 \cdot 0,4 \mu\text{T} \cdot 300 \text{ V/T} = 0,24 \text{ V}$$

$$U_{12} = \frac{U_1 + U_2}{2} = B_S S + U_{\text{ref}} = 2,8 \text{ V}$$

$$U_{12} = A_D \cdot U_D \pm A_Z \cdot U_Z = 2,4 \text{ V} \pm 280 \mu\text{V}$$

4.5. OPTIČKI SENSOR (fotodioda)

→ za mjerjenje udaljenosti i koristimo diodu i fotodiodu

[ODAŠTAČ] [PRIJEMNIK]

upadus zračenje $E_0 = 1 \text{ mW/cm}^2$

$V=0 \text{ V} \rightarrow I = 40 \mu\text{A}$

$I_E = 40 \text{ mW sr}^{-1}$ pri istosmernoj strji $I_F = 250 \text{ nA}$;

$U_F = 1,2 \text{ V}$

NA RASPRAVljaju:


$2 \times R$

O.P.

$U = 15 \text{ V}$

$U_{12} = 10 \text{ V}, r = 1 \text{ cm}$

$r = 10 \text{ cm}, U_{12} = ?$

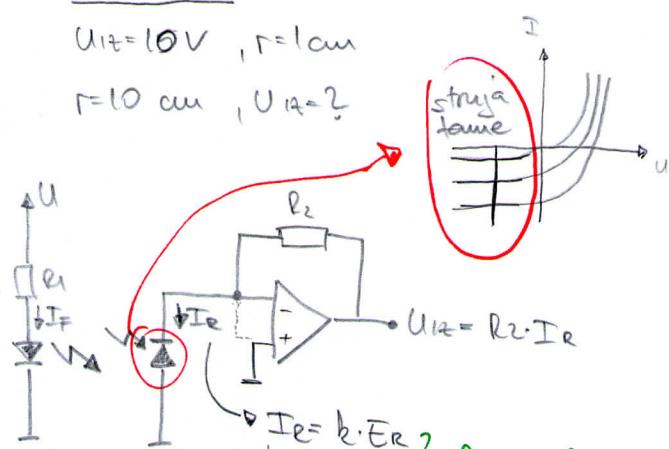

$$R_1 = \frac{U - U_F}{I_F} = 55,2 \Omega$$

$$E_R = \frac{I_E}{r^2}, \beta = \phi$$

$$U_{12} = R_2 \cdot I_E \Rightarrow I_E = \frac{U_{12}}{R_2}$$


$$R_2 = \frac{U_{12} \cdot r^2}{k \cdot I_E} = [U_{12} = 10, r = 1 \text{ cm}]$$

$$= \frac{10 \text{ V} \cdot 1 \text{ cm}^2}{40 \mu\text{A} \cdot 40 \text{ mW sr}^{-1}} = 6250 \Omega$$

$$R_2 = 6250 \Omega, r = 10 \text{ cm} \Rightarrow U_{12} = \frac{R_2 \cdot k \cdot I_E}{r^2}$$

$$U_{12} = 0,1 \text{ V}$$

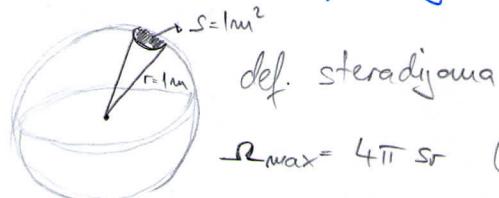* najvećije fizikalne veličine u optoelektroničkim aplikacijama



$\Omega_{max} = 4\pi \text{ sr}$ (* jer je površina sfere $4\pi r^2$)

PROSTORNI KUT

$$\Omega = \frac{S}{r^2}$$

$$\text{dif. oblik} \rightarrow d\Omega = \frac{1}{r^2} d\vec{S} \cdot \vec{r}$$

INTENZITET ZRACENJA

$$I = \frac{d\Phi}{d\Omega} \rightarrow \text{snaga ili tok zračenja}$$


GUSTOĆA UPADNOG ZRACENJA

$$E = \frac{d\Phi}{dS} \quad [\text{W/m}^2]$$

* ZA TOČKASTI IZVOR

$$d\Phi = \frac{I}{r^2} \cos(\beta) dS$$

$$E = \frac{I \cos(\beta)}{r^2}$$

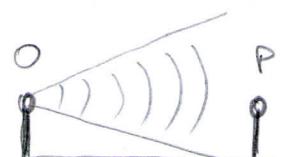

$\cos \beta$
čovjet pod
kojim je
ugnut
prizemnik


* also su diode mrežnjakom
zadivljene za kut β , odnos
između stvarne udaljenosti i
udaljenosti dobivene na ovaj način γ :

$$\Gamma_{mrežnjak} = \frac{1}{\sqrt{\cos \beta}} \Gamma_{stvarno}$$

5. POJĀČALA

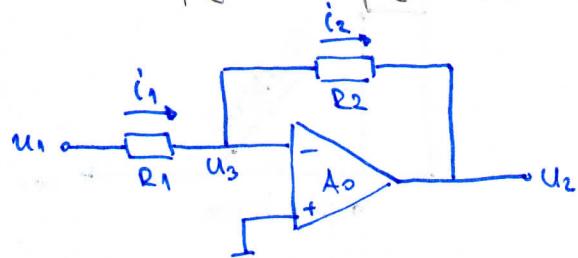5.1. INVERTIRAJUĆE POJĀČALO

→ Izvesti pojāčalo s pojāčanjem -10 i $R_{ul} = 10 \text{ k}\Omega$



* Zamjenimo struje kroz vodice u. O.P.

$$\frac{U_1 - U_3}{R_1} = \frac{U_3 - U_2}{R_2}$$

$$U_2 = A_o \cdot (U_+ - U_-) = -A_o \cdot U_2 \Rightarrow U_3 = -\frac{U_2}{A_o}$$

$$\frac{U_1 + \frac{U_2}{A_o}}{R_1} = \frac{-\frac{U_2 - U_2(A_o)}{A_o}}{R_2} / R_1 R_2$$

$$R_2 \left(\frac{U_1 A_o + U_2}{A_o} \right) = R_1 \cdot \left(\frac{-U_2 - U_2(A_o)}{A_o} \right)$$

$$R_2 A_o \cdot U_1 + R_2 U_2 + R_1 U_2 + R_1 A_o U_2 = 0$$

$$U_1 (R_2 A_o) = -U_2 (R_2 + R_1 + R_1 A_o)$$

$$\frac{U_2}{U_1} = \frac{-R_2 A_o}{R_2 + R_1 + R_1 A_o} = -\frac{R_2}{R_1} \cdot \frac{A_o}{1 + \frac{1}{A_o} \cdot \left(1 + \frac{R_2}{R_1} \right)}$$

$$A_{inv} = -\frac{R_2}{R_1} \cdot \frac{1}{1 + \frac{1}{A_o}}$$

odstupanje
z bog konacnog
pojacaanja

$$\epsilon = \frac{1}{\beta A_o}, \beta = \frac{R_1}{R_1 + R_2}$$

orisi o frekvenciji \rightarrow NF $A_o \rightarrow \infty$
VF A_o pada 20 dB/doble

* ULATNI OTPOR NEINVERTIRAJUĆEG POJĀČALA

$\neq R_1$


$$R_{ul} = \frac{U_1}{i_1} = R_1 = 10 \text{ k}\Omega \Rightarrow A_{inv} = -10 = -\frac{R_2}{R_1} \Rightarrow R_2 = 100 \text{ k}\Omega$$

5.2. utjecaj unutarnjeg otpora generatora na pojāčanje

→ Izvesti pojāčalo koje će invertirati naponski signal generatora?

$$R_{ul} = 10 \text{ k}\Omega$$

$$R_{1+} = 1 \text{ k}\Omega$$

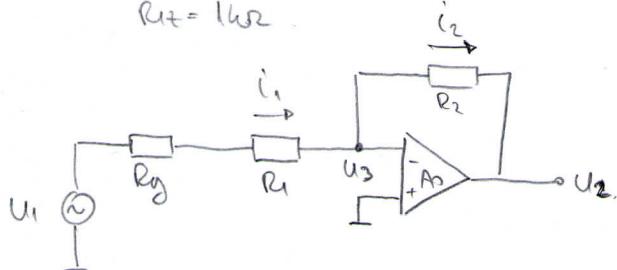

$$A_{inv} = -\frac{R_2}{R_1 + R_g}$$


$$R_{ul} = R_1 = 10 \text{ k}\Omega$$

$$R_1 + R_g = 11 \text{ k}\Omega$$

velika razlika !

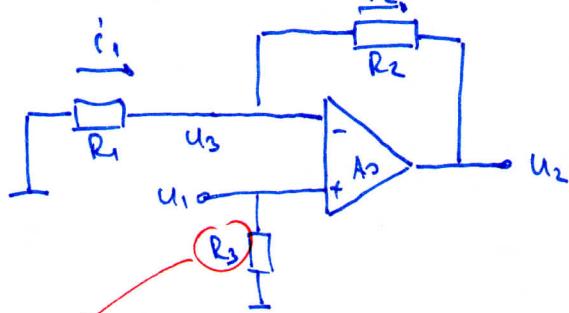5.3. NEINVERTIRAJÚCE POJÁCIALO

→ prijmeniam O.P. závesi pojáca s pojácaním +10 : $R_{ul} = 10 \text{ k}\Omega$



R_3 je vlastnú odpor neinvertujúceho pojáčala

↳ pravilo : $R_3 = R_1 \parallel R_2 \rightarrow$ tento smyslujeme napäťovou posuvku Δ



$$\frac{\phi - u_3}{R_1} = \frac{u_3 - u_2}{R_2}$$

$$|u_2 = A_o(u_1 - u_3)| \rightarrow \text{zraz za koviacom } A_o$$

$$\hookrightarrow u_3 = -\frac{u_2}{A_o} + u_1 \Rightarrow A_{mehr} = \left(1 + \frac{R_2}{R_1}\right) \frac{1}{1 + \frac{1}{A_o} \left(1 + \frac{R_2}{R_1}\right)} = \boxed{\left(1 + \frac{R_2}{R_1}\right) \frac{1}{1 + \varepsilon}}$$

$$A_{mehr} = 10 = 1 + \frac{R_2}{R_1} \Rightarrow \boxed{R_2 = 9R_1}$$

$$R_{ul} = R_3 = \frac{R_1 \cdot R_2}{R_1 + R_2} = 10 \text{ k}\Omega \Rightarrow \frac{9R_1}{10R_1} = 10 \text{ k}\Omega \Rightarrow R_1 = \frac{10 \cdot 10}{9} = 11,111 \text{ k}\Omega$$

$$R_2 = 99,9999 \text{ k}\Omega$$

* v praxi nemôžeme pravci telove odpory po se kovisti potenciometrom


5.6. DIFERENCIJALNO POJĀČALO IZUEDENO JEDNIM O.P.

$$A_D = 10$$

$$R_{ul_D} = 20 \text{ k}\Omega$$

$$F_{0P} = \underline{60 \text{ dB}}$$

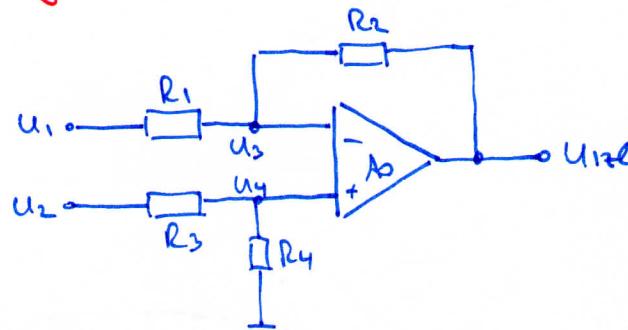otpornici savršeno
upareni osim jednog
koji odstupa:



- a) 0,1%
 - b) 1%

$$U_{1,2,3} = \left(1 + \frac{R_2}{R_1}\right) \left(\frac{R_4}{R_3 + R_4}\right) \cdot U_2 - \frac{R_2}{R_1} U_1$$

invertingiųjė · potencijal
U₄

neinvertingiųjė

$$\underline{\text{IZVOD}}: \quad \left. \begin{array}{l} U_D = U_2 - U_1 \\ U_2 = \frac{U_2 + U_1}{2} \end{array} \right\} \Rightarrow \quad \begin{array}{l} U_1 = U_2 - \frac{U_D}{2} \\ U_2 = U_2 + \frac{U_D}{2} \end{array}$$

$$\begin{aligned}
 U_{12l} &= \left(1 + \frac{R_2}{R_1}\right) \left(\frac{R_4}{R_3 + R_4}\right) \left[U_2 + \frac{U_D}{2}\right] - \frac{R_2}{R_1} \left[U_2 - \frac{U_D}{2}\right] \\
 &= \frac{U_D}{2} \left[\frac{R_1 + R_2}{R_1} \cdot \frac{R_4}{R_3 + R_4} + \frac{R_2}{R_1} \right] \pm U_2 \left[\frac{R_1 + R_2}{R_1} \frac{R_4}{R_3 + R_4} - \frac{R_2}{R_1} \right] \\
 &= \frac{U_D}{2} \left[\frac{R_1 R_4 + R_2 R_4 + R_2 R_3}{R_1 (R_3 + R_4)} \right] \pm U_2 \left[\frac{R_1 R_4 + R_2 R_4 - R_2 R_3 - R_1 R_4}{R_1 (R_3 + R_4)} \right] \\
 &= \frac{1}{2} \cdot \underbrace{\left[\frac{R_1 R_4 + R_2 R_3 + 2 \cdot R_2 R_4}{R_1 R_3 + R_1 R_4} \right]}_{A_D} U_D \pm \underbrace{\left[\frac{R_1 R_4 - R_2 R_3}{R_1 R_3 + R_1 R_4} \right]}_{A_2} U_2 \\
 &= A_D \cdot U_D \pm A_2 \cdot U_2
 \end{aligned}$$

• VÁZNO

→ IDEALNO DIF. PRACTICO : $A_0 > 0$; $A_2 = 0 \Rightarrow$ da bi to vymedilo množstvo bití:

also to prove the validity

$$R_1 \cdot R_4 = R_2 \cdot R_3 \quad , \quad \begin{cases} R_1 = R_3 \\ R_2 = R_4 \end{cases} \} \text{prawie}$$

$$\text{Ad idealus} = \frac{R_2}{R_1}$$

A₂ ideals = Ø

$$\text{faktor protislivnja (CMRR)} \Rightarrow F_R = \left| \frac{A_D}{A_2} \right| = \frac{R_1 R_4 + R_2 R_3 + 2 R_2 R_4}{2 |(R_1 R_4 - R_2 R_3)|}$$

$\approx 100 \text{ dB}$

$$F = \frac{F_{op} F_R}{F_{op} + F_R} \quad (\text{ovdje se uočavaju absolutni brojevi})$$

$$R_{ul,D} = R_1 + R_3 \quad , \quad R_1 = R_3 \Rightarrow R_{ul,D} = 2R_1$$

$$f_{\text{filter}} = 20 \text{ Hz} \Rightarrow R_1 = R_3 = 10 \text{ k}\Omega$$

$$A_{\text{ideal}} = 10 = \frac{R_2}{8} \Rightarrow R_2 = R_4 = 100 \text{ k}\Omega$$

* razlika also se jedan otpornih
precinjeni i u skripti

5.7. SPOJ DIF. POJАČALA I OTPORNIČKOG MOSTA


$$R_1 = R_2 = 10 \text{ k}\Omega$$

$$R_3 = R_4 = 100 \text{ k}\Omega$$

$$F_{op} = 62 \text{ dB}$$

$$R = 1 \text{ k}\Omega$$

$$R_T = 1.5 \text{ k}\Omega$$

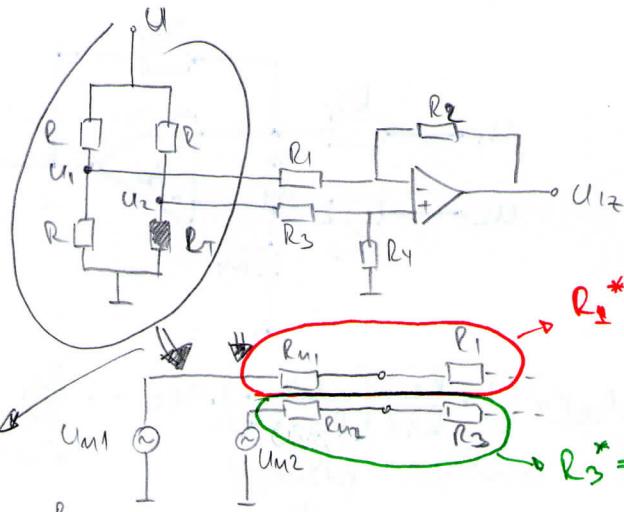

$$R_1^* = R_1 + R_{M1}$$

$$R_3^* = R_3 + R_{M2}$$

$$U_{M1} = U \cdot \frac{R}{R+R} = \frac{U}{2} \quad R_{M1} = R || R = \frac{R}{2} = 500 \text{ }\Omega$$

$$U_{M2} = U \cdot \frac{R_T}{R_T+R} = \frac{3}{5}U \quad R_{M2} = \frac{R_T \cdot R}{R_T+R} = 600 \text{ }\Omega$$

$$\boxed{R_1^* \neq R_3^*} \rightarrow \text{nesarisseost otporničke mreže} \Rightarrow A_0 = \frac{R_1 R_4 + R_2 R_3 + 2 R_2 R_4}{2(R_1 R_3 - R_1 R_4)} = 9,5195 \quad (10)$$


$$|A_z| = \left| \frac{R_1 R_4 - R_2 R_3}{R_1 R_3 + R_1 R_4} \right| = 8,611 \cdot 10^{-3} \quad (11)$$

$$F_{mest} = \frac{A_0}{|A_z|} = 1105,5 \quad (\infty)$$

$$F_{ulupos} = \frac{F_{op} \cdot F_{mest}}{F_{op} + F_{mest}} = 525 \Rightarrow 54,4 \text{ dB}$$


5.8. INSTRUMENTACIJSKO POJĀČALO

I. STUPANJ

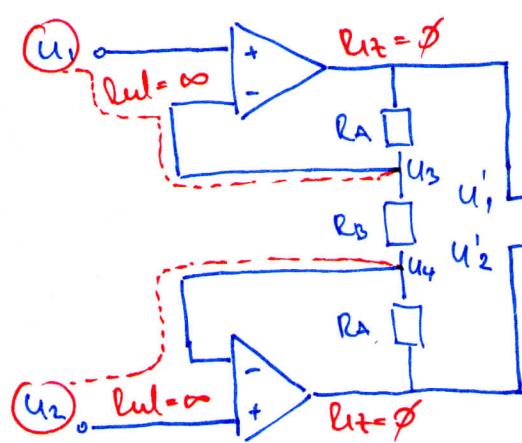

II. STUPANJ

klasično dif. pojāčalo

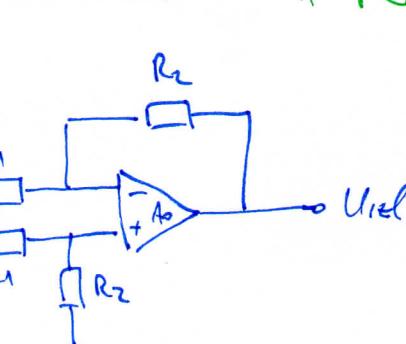

idealno

IZVOD:

$$\frac{U_1' - U_3}{R_A} = \frac{U_3 - U_4}{R_B}$$

$$\frac{U_3 - U_4}{R_B} = \frac{U_4 - U_2'}{R_A}$$

$$U_1 = U_3 \quad [\text{zbog velikog pojāčanja}]$$

$$U_2 = U_4$$

izvod za
I. stupanj

$$\frac{U_1' - U_1}{R_A} = \frac{U_1 - U_2}{R_B} \Rightarrow U_1' = \frac{R_A}{R_B}(U_1 - U_2) + U_1 \Rightarrow U_1' = -\frac{R_A}{R_B}(U_2 - U_1) + U_1$$

$$\frac{U_1 - U_2}{R_B} = \frac{U_2 - U_2'}{R_A} \Rightarrow U_2' = -\frac{R_A}{R_B}(U_1 - U_2) + U_2 \Rightarrow U_2' = \frac{R_A}{R_B}(U_2 - U_1) + U_2$$

→ II. stupanj

→ idealan pojāčava samo dif. napr., $A_{2z} = 0$

$$U_2' - U_1' = 2 \frac{R_A}{R_B}(U_2 - U_1) + U_2 - U_1 = \underbrace{\left(1 + \frac{2R_A}{R_B}\right)}_{\text{dif. napr na ulazu u II. stupanj}} \cdot (U_2 - U_1) \rightarrow \text{dif. napr na ulazu u II. stupanj}$$

A II. STUPANJ JE ZAPRAVO DIF. POJĀČALO PA:

$$U_{1z} = \left(1 + \frac{2R_A}{R_B}\right) \frac{R_2}{R_1} (U_2 - U_1) \rightarrow \text{dif. napr na ulazu pojāčala}$$

$$A_{D, \text{ustr}} = \left(1 + \frac{2R_A}{R_B}\right) \frac{R_2}{R_1}$$


↪ valazi se van čipa te nijeme manjestano
pojāčanje

5.9. ZADACI

$$\textcircled{3} \quad R_1 = R_2 = R_3 = 2 \text{ M}\Omega$$

$$R_4 = 27,4 \text{ k}\Omega$$

$$A = ? , U_{\text{ul}} = ?$$

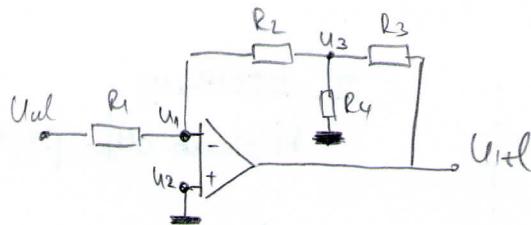

$$R_{\text{ul}} = R_1 = 2 \text{ M}\Omega$$

$$A = \frac{U_{\text{ul}}}{U_{\text{ul}}} , \quad U_1 = U_2 = \emptyset$$

$$\textcircled{1} \quad \frac{U_{\text{ul}} - U_1}{R_1} = \frac{U_1 - U_3}{R_2} \Rightarrow \frac{U_{\text{ul}}}{R_1} + \frac{U_3}{R_2} = \emptyset \Rightarrow U_3 = -\frac{R_2}{R_1} \cdot U_{\text{ul}}$$


$$\textcircled{2} \quad \frac{U_1 - U_3}{R_2} = \frac{U_3}{R_4} + \frac{U_3 - U_{\text{ul}}}{R_3} \Rightarrow \frac{U_3}{R_4} + \frac{U_3}{R_2} + \frac{U_3 - U_{\text{ul}}}{R_3} = 0 \Rightarrow -\frac{R_2}{R_1 R_4} U_{\text{ul}} - \frac{1}{R_1} U_{\text{ul}} - \frac{R_2}{R_1 R_3} U_{\text{ul}} - \frac{1}{R_3} U_{\text{ul}} = \emptyset$$

$$U_{\text{ul}} \left(-\frac{R_2}{R_1 R_4} - \frac{1}{R_1} - \frac{R_2}{R_1 R_3} \right) = \frac{1}{R_3} U_{\text{ul}}$$

$$\frac{U_{\text{ul}}}{U_{\text{ul}}} = A = R_3 \cdot \left(-\frac{R_2}{R_1 R_4} - \frac{1}{R_1} - \frac{R_2}{R_1 R_3} \right) = \underline{\underline{-75}}$$

$$\textcircled{4} \quad A_D = 100$$
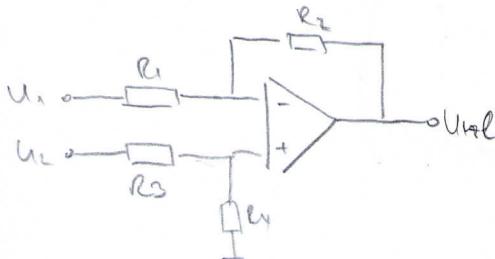
$$\boxed{R_2^* = 1.01 \cdot R_2} \Rightarrow A_D' = ? , F = ?$$



* idealno \Rightarrow

$$R_1 = R_3$$

$$R_2 = R_4$$

$$U_{\text{ul}} = \left(1 + \frac{R_2}{R_1} \right) \cdot \frac{R_4}{R_3 + R_4} \cdot U_2 + \frac{R_2}{R_1} U_1$$

$$\begin{aligned} U_0 &= U_2 - U_1 \\ U_2 &= \frac{U_1 + U_2}{2} \end{aligned} \Rightarrow \begin{aligned} U_1 &= U_2 - \frac{U_0}{2} \\ U_2 &= U_2 + \frac{U_0}{2} \end{aligned}$$

$$U_{\text{ul}} = \left[\frac{R_1 R_4 + R_2 R_3 + 2 R_2 R_4}{2(R_1 R_3 + R_1 R_4)} \right] U_0 + \left[\frac{R_1 R_4 - R_2 R_3}{R_1 R_3 + R_1 R_4} \right] U_2$$

(Ad)

A₂

$$A_{\text{D}, \text{idealno}} = \frac{R_2}{R_1} = 100$$

$$\boxed{A_{\text{D}}^* = 1.01 \cdot 100 = 101}$$

$$|A_2| = \sqrt{\frac{100 R_2^2 + 101 R_1^2}{R_1^2 + 100 R_2^2}} = 0,10099$$

$$F = \frac{A_{\text{D}}^*}{A_2} = 10201 \Rightarrow \underline{\underline{80,17 \text{ dB}}}$$

6) teztometri

$$R = 350 \Omega$$


$$k = 2$$

$$U = 10 V$$

$$F_{op} = 100 dB$$

$$\text{bez mesta} \Rightarrow R_{ul,D} = 7 k\Omega, A_D = 10$$


a) uvačtati obř. pojednalo

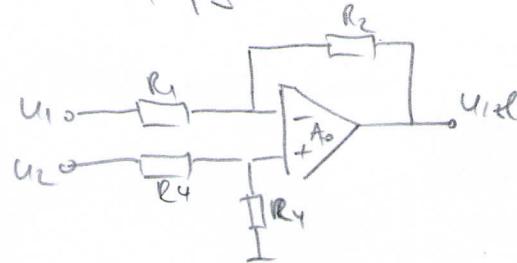

$$R_{ul,D} = 7 k\Omega = 2 R_1 \Rightarrow R_1 = 3,5 k\Omega = R_3$$

$$A_D \text{ideal } \omega = 10 = \frac{R_2}{R_1} \Rightarrow R_2 = R_4 = 35 k\Omega$$

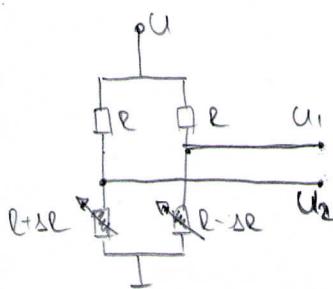
b) teztometri $sl = 1\%$, $A_D, A_Z, F = ?$



teztometri:

$$\frac{\frac{\Delta R}{R}}{\frac{sl}{l}} = k \Rightarrow \frac{\frac{\Delta R}{350}}{\frac{0,01\ell}{\ell}} = 2 \Rightarrow \Delta R = 7 \Omega \rightarrow R + \Delta R = 357 \Omega$$

$$R - \Delta R = 343 \Omega$$

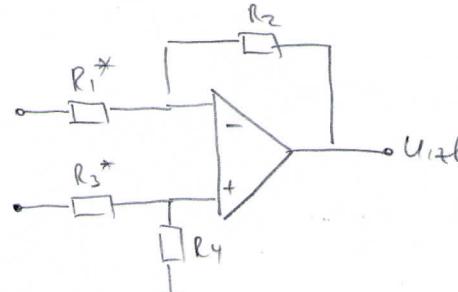

$$R_1^* = R_1 + R_x = \underline{\underline{367,73 \Omega}}$$

$$R_3^* = R_3 + R_y = \underline{\underline{3673,23 \Omega}}$$

$$R \parallel (R + \Delta R) = 176,73 \Omega = R_x$$

$$R \parallel (R - \Delta R) = 173,23 \Omega = R_y$$

$$U_1 = U \cdot \frac{R - \Delta R}{R + R - \Delta R} = 4,95 V$$

$$U_2 = U \cdot \frac{R + \Delta R}{R + R + \Delta R} = 5,05 V$$

$$U_d = \frac{U_1 + U_2}{2} = 5 V$$

$$U_d = U_2 - U_1 = 0,1 V$$

$$U_{1,el} = \left(1 + \frac{R_2}{R_1} \right) \frac{R_4}{R_3 R_4} U_2 + \frac{R_2}{R_1} U_1$$

$$= \underbrace{\left(\frac{R_1 R_4 + R_2 R_3 + 2 R_2 R_4}{2 \cdot (R_1 R_3 + R_1 R_4)} \right) U_d}_{A_D} \pm \underbrace{\left(\frac{R_1 R_4 - R_2 R_3}{R_1 R_3 + R_1 R_4} \right) U_2}_{A_Z}$$

$$A_D = \frac{R_1^* R_4 + R_2 R_3^* + 2 R_2 R_4}{2 \cdot (R_1^* R_3^* + R_1^* R_4)} = 9,52$$

$$A_Z = \frac{R_1^* R_4 - R_2 R_3^*}{R_1^* R_3^* + R_1^* R_4} = 8,62 \cdot 10^{-4}$$

$$F_e = \left| \frac{A_D}{A_Z} \right| = 11050,27$$

$$F = \frac{F_{op} \cdot F_e}{F_{op} + F_e} = 9850,69 \Rightarrow 80 dB$$

⑧ instrumentacijos pajėgos


ukupno pajėgos $< 30 - 310 >$

II. stupaij $R_{ul,D} = 10 \text{ k}\Omega$

$$A_D = 10$$

$$F = \infty$$

I. stupaij

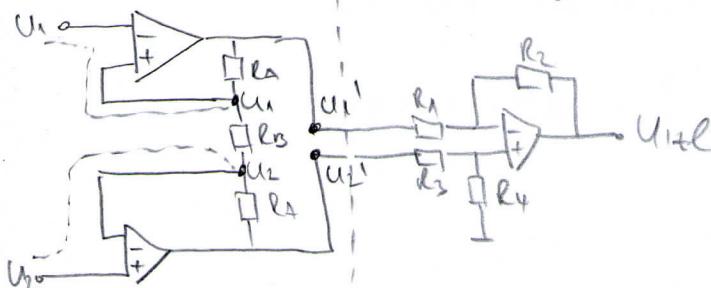

II. stupaij

II. stupaij

$$A_{D,idealuo} = \frac{R_2}{R_1} = 10 \Rightarrow R_2 = 10R_1 = 500 \text{ k}\Omega = R_3$$

$$R_{ul,D} = 2R_1 \Rightarrow R_1 = 50 \text{ k}\Omega = R_3$$

I. stupaij

$$\frac{U_1' - U_1}{R_A} = \frac{U_1 - U_2}{R_B} \Rightarrow U_1' = -\frac{R_A}{R_B}(U_2 - U_1) + U_1 \quad \left. \right\}$$

$$\frac{U_1 - U_2}{R_B} = \frac{U_2 - U_1'}{R_A} \Rightarrow U_1' = \frac{R_A}{R_B}(U_2 - U_1) + U_2 \quad \left. \right\}$$

$$\begin{aligned} U_d &= U_2 - U_1' = 2 \cdot \frac{R_A}{R_B}(U_2 - U_1) + U_1 + U_2 \\ &= \left(1 + 2 \frac{R_A}{R_B}\right)(U_2 - U_1) \end{aligned}$$

$$A_{D,instrumentacijos} = \left(1 + 2 \frac{R_A}{R_B}\right) \frac{R_2}{R_1}$$

$$30 = \left(1 + 2 \cdot \frac{R_A}{10}\right) \cdot 10 \Rightarrow R_A = 10 \text{ k}\Omega$$

$$R_B < 0,67, 10 \text{ k}\Omega$$

$$310 = \left(1 + 2 \cdot \frac{10}{R_B}\right) \cdot 10 \Rightarrow R_B = 0,67 \text{ k}\Omega$$